

COMPOUND CIRCUIT

1. What is the current in amps through the battery?
2. What is the current in amps through the pair of 10 ohm resistors?
3. What would it be through the 8 ohm resistors?
4. What is the power supplied by the battery?

